

# WORKSHEET

## SERIES P9

Student Name \_\_\_\_\_ date \_\_\_\_\_ MB# \_\_\_\_\_

Students should be able to Calculate, Measure and Compare fundamental characteristics of a series circuit.

- **Measure:** The student will use a Digital Multimeter (DMM), to measure the current (I), voltage (E), and resistance (R) for the Circuit on the P9 circuit on the Miniboard Series Trainer (simulator).
- **Calculate:** The student will use the principles of ohms law to calculate, current (I), voltage (E), and resistance R for the P9 Circuit using the measurements taken with the DMM on the Miniboard Series Trainer (simulator).
- **Compare:** The student will then compare the results of the measurements taken and those calculated using the DMM measurements to calculate.

### Part A Measure

#### Measuring Voltages:

Measure and record Battery Voltage a \_\_\_\_\_

Measure and record Voltage Drop for resistor R1 b \_\_\_\_\_

Measure and record Voltage Drop for resistor R2 c \_\_\_\_\_

Measure and record Voltage Drop for resistor R3 d \_\_\_\_\_

Measure and record Voltage Drop for resistor R4 e \_\_\_\_\_

Measure and record Total Voltage Drop for series circuit P9 f \_\_\_\_\_

#### Measuring Resistance:

Measure and Record resistance of resistor R1 g \_\_\_\_\_

Measure and Record resistance of resistor R2 h \_\_\_\_\_

Measure and Record resistance of resistor R3 i \_\_\_\_\_

Measure and Record resistance of resistor R4 j \_\_\_\_\_

Measure and Record total resistance (Rt) or circuit P9 k \_\_\_\_\_

#### Measuring Amperage

Measure and Record the amperage of circuit P9 l \_\_\_\_\_

## Part B Calculate

### **Calculate Voltage (IXR)**

Calculate Voltage Drop by multiplying resistance x amperage for each resistor.

R1 voltage drop (g x l) m\_\_\_\_\_

R2 voltage drop (h x l) n\_\_\_\_\_

R3 voltage drop (i x l) o\_\_\_\_\_

R4 voltage drop (j x l) p\_\_\_\_\_

Circuit P9 Total voltage drop (m +n + o + p) Sum q\_\_\_\_\_

Circuit P9 Total voltage drop Calculated (k x l) r\_\_\_\_\_

### **Calculate Resistance (E/I)**

Calculate Resistance by dividing voltage by amperage.

R1 Resistance (b / l) s\_\_\_\_\_

R2 Resistance (c / l) t\_\_\_\_\_

R3 Resistance (d / l) u\_\_\_\_\_

R4 Resistance (e / l) v\_\_\_\_\_

Circuit P9 (Rt) Resistance Total Sum w\_\_\_\_\_

Circuit P9 Calculated Resistance Total (f / l) x\_\_\_\_\_

### **Calculate Amperage (E/R)**

Circuit P9 (It) Amperage Total (f / k) y\_\_\_\_\_

## **Part C Compare**

Record measured and calculated results to complete the following table. Note: letters in each cell refer to your answers above. (Measured and calculated readings should be less than  $\pm 5\%$ )

Voltages	Measured	Calculated		< 5% difference Y /N
R1 voltage drop	b	m		
R2 voltage drop	c	n		
R3 voltage drop	d	o		
R4 voltage drop	e	p	<b>Voltage Drop Sum</b>	
P9 total voltage drop	f	r	q	
Resistance	Measured	Calculated		
R1 resistance	g	s		
R2 resistance	h	t		
R3 resistance	i	u		
R4 resistance	j	v	<b>Resistance Sum</b>	
P9 resistance total (Rt)	k	x	w	
Amperage	Measured	Calculated		
P9 circuit amperage	l	y		